

1. b, c

2. A

\$zero 只读不可写, 能被任何数整除.
\$sp 可以加 1, 加 2, 不一定只加 4.

3. a.

4. a, b, c

b, c 包含在 a 里面

5. cause overflow?

D

zero extension & ones extension 包含在 sign extension 里.
进位不一定代表 overflow, (c): $1111 + 0001 = 0000$
 $-1 + 1 = 0$
b) = -8 c) = 0 a) ok. d) = 8 (-8 ~ 7)

6. 16

7. B

2^{16} 个 instruction $\Rightarrow 2^{18}$ bytes.

opcode 6 - rs 5 - rt 5 - imm 16

signed 16 bit $[-2^{15} \sim 2^{15}-1]$ 2^{16} 个数 $\Rightarrow 2^{16}$ instruction $\Rightarrow 2^{18}$ byte

★ branch 都是 i-type

8. D 2^{28}

9. high-z

10. 256 B

6 address $\Rightarrow 2^6$ 个 instruction \Rightarrow Memory = $2^6 \cdot 4B$
32 bit $\Rightarrow 4$ Bytes $\Rightarrow 2^8 B$
 $= 256 B$

11. 8 bits

memory = 1024 B. \Rightarrow instruction = $\frac{1024 B}{4 B} = 256 \Rightarrow \log_2(256) = 8$
32-bit = 4 B.

12. x: 16

y: 1

if n bits number \rightarrow shift register take n clock cycles
load register take 1 clock cycles.

13. 对 bge

#slt d s t \Rightarrow if $s < t$:
d = 1

a b
c d

a) \checkmark


b) \times

c) \times

d) \checkmark

#bne 和 beq 条件相反.

14. b.

15. 

$$15 = 8 + 4 + 2 + 1$$



2-1 Mux 用 4

3-1 Mux 用 2 : $3 = 2 + 1$

4-1 Mux 用 : $4 = 2 + 2$

5-1 Mux : $5 = 2 + 2 + 1$
 $= 4 + 1$

6-1 Mux : $6 = 4 + 2$

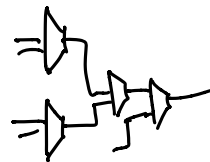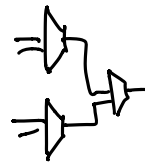

16 B. D

$$b) = x\bar{y}z + x\bar{y}\bar{z} = x\bar{y}$$

17.

Matal 1


Oxide 3

Semi 2

18. 略

19. package 同

20. i) moore machine
输出不能状态有关

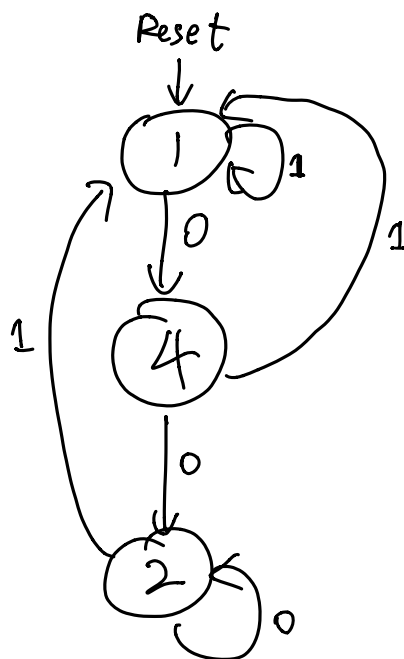

ii) 写 2 个 模块.



iii) 4.

iv) (6)

part C: 1. Booth's alg

$$A = -5 \quad B = -7$$

$$1. \quad A' = 10 \Rightarrow \text{minus.}$$

$$\begin{array}{r} 0000 \ 0000 \\ + \ 0011 \\ \hline P = 0111 \ 0000 \end{array}$$

$$P \gg 1 \Rightarrow 0011 \ 1000$$

$$A' = 11011$$

$$2. \quad A' = 11 \Rightarrow \text{shift}$$

$$P \gg 1 = 0001 \ 1100$$

$$A' \gg 1 = 11100$$

$$3. \quad A' = 01 \text{ add}$$

$$\begin{array}{r} 0001 \ 1100 \\ + \ 1001 \\ \hline P = 1010 \ 1100 \end{array}$$

$$P \gg 1 = 1101 \ 0110$$

$$A' \gg 1 = 11110$$

$$4. \quad A' = 10 \text{ minus}$$

$$\begin{array}{r} 1101 \ 0110 \\ - \ 0111 \\ \hline P = 1101 \ 0110 \end{array}$$

$$P \gg 1 = 0010 \ 0011_{(2)} = 35_{(10)}$$

$$2. \quad a) \quad PC := \$ra + \$zero$$

$$b) \quad \$ra := PC$$

c)

$$1) \quad D \quad \boxed{100011} \quad \begin{array}{c} rs \\ 11101 \\ \hline 29 \end{array} \quad \begin{array}{c} t \\ 00010 \\ \hline 2 \end{array} \quad \left| \quad \begin{array}{c} imm \\ 1111 \dots 1111 \\ \hline 16 \end{array} \right.$$

lw, \$0, -((\$sp)

$$vi) \quad C \quad \begin{array}{l} 30 = 000 \dots 011110 \\ -30 = 111 \dots 100010 \end{array}$$

$$\boxed{100/00} \overset{8}{0/000} \overset{9}{0/001} \mid 111 \dots 111000/0$$

-30

1bu $\$t_1$, -30($\t_0)

iii)

F

6143

2 | 6143

2 | 3071

2 | 1535

2 | 767

2 | 383

2 | 191

2 | 95

2 | 47

2 | 23

2 | 11

2 | 5

2 | 2

2 | 1

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

0

00000

00000

00000

00000

v.)

B

$$\overset{2}{00010} \mid \dots$$

iv)

A

$$\begin{array}{ccc} d & s & t \\ \$t_8 & \$t_0 & \$t_1 \\ 0/000 & 0/001 & \dots \end{array}$$

ii)

E

2. a) $\$sp := \$sp + 4(\text{imm})$

0	0	x	0	0
0	0	xx	001	
1	10	1	0	

b) $\$ra := PC + 100$

0	0	x	0	0
0	0	xx	001	1011
0	10	1	0	

↑
从PC来的
所以是"0"

c)

0	0	0	1	0
x	1	xx	xxx	
x	xx	0	x	

Fetch 读-个东西

Part 1:

32-bit instruction register which can decode the input message into opcode, rs, rt, rd, and imm

1. i: imm
0: opcode

3. reg [3:0] M [255:0]
⇒ 53-个RAM

Input [7:0] a ; \rightarrow address

answer :

create a $256 * 4$ bit RAM
with synchronous enable
with one-bit wire signal w that control
write or read

4. e = enable
w = write/read'

part F

1. a) sra \$s0, \$s0, 3

b) xori \$a0, \$a0, -1

c) # ~~is~~ load 指令
lb \$t0, 0(\$sp)

★ d) # ~~is~~ pc = 0

jr \$zero
r-type

better

j 0
j-type

\Rightarrow 只影响后 26 位
高 6 位无法改